Sensors, Signals and Noise

COURSE OUTLINE

- Introduction
- Signals and Noise
- Filtering: LPF2 Switched-Parameter Filters
- Sensors and associated electronics

- Switched-parameter RC low-pass filters
- Sample and Hold S&H
- Gated Integrator GI

Switched-parameter RC low-pass filters

Switched-parameter RC low-pass filters



- State with S down (closed in short circuit): the circuit behaves like a constant-parameter RC integrator; current can flow in and out of C
- State with S up (open circuit): the circuit is in HOLD, no current can flow, the charge previously stored in C is maintained, the voltage on C stays constant.

In the cases here considered: (a) the initial state is with *S* open and zero charge in C (b) the command closes *S* in synchronism with the signal to be acquired and re-opens S after the acquisition

Switched-parameter RC low-pass filters



5

Sample and Hold S&H

Sample and Hold (S&H)



The S&H has unity DC gain (C is fully charged at the input voltage within T_G)

$$W_m(0) = \int_0^\infty w_m(\alpha) d\alpha = 1$$

The S&H has very mild filtering action, equivalent to that of a constant-parameter RC integrator with equal time constant T_{fS} . With wide-band input noise S_b (bilateral)

$$\overline{y_n^2} = S_b \cdot \frac{1}{2T_f}$$

Real vs ideal S&H



- The minimum available T_f is limited by the technology of devices and circuits (finite R values of fast switching devices and C values required for holding information)
- S&H acquisition time = time for reaching the full output value ≈ a few T_f, i.e. currently some tens of nanoseconds in discrete-component circuits some tens of picoseconds in integrated circuits with minimized capacitances

S&H equivalent model



S&H Readout Noise

- **READOUT NOISE** of a sampling circuit is the contribution to the output noise due to the internal noise sources in the sampling circuit itself
- In the S&H the main source of readout noise is the wide-band Johnson noise of R with spectral density $S_{bB} = 2kTR$ (bilateral)

Since

$$w(\alpha) = \frac{1}{T_f} e^{-\frac{(t_m - \alpha)}{T_f}} 1(t_m - \alpha) \text{ and } k_{ww}(\tau) = \frac{1}{2T_f} e^{-\frac{|\tau|}{T_f}}$$

the readout noise is



this is just the noise generated and self-filtered by a constant parameter RC filter and is INDEPENDENT OF THE R VALUE, in agreement wth the S&H circuit model.

Gated Integrator GI

Gated Integrator (GI)



- For behaving as GI (uniform weight in T_G) the circuit must have $T_f >> T_G$
- Therefore, the DC gain G is inherently much less than unity

$$G = W_m(0) = \int_0^\infty w_m(\alpha) d\alpha = \frac{T_G}{T_f} \ll 1$$

- A GI has remarkable filtering action on a wide-band input noise, that is, on noise with autocorrelation width much shorter than the gate duraton T_G .
- Long gate duration T_G is well feasible in practice, much better than a long averaging interval T_a in a mobile-mean filter

Gated Integrator (GI)

TIME DOMAIN

FREQUENCY DOMAIN



Filtering and S/N enhancement by GI

INPUT:

- signal x_s constant in T_G (DC signal)
- wide-band noise S_b (bandwidth $f_n >> 1/T_G$ and autocorrelation width $T_n << T_G$) $x_n^2 = S_h^2 f_n = S_h^2 / 2T_n$

OUTPUT:

Signal
$$y_s = x_s \cdot \frac{T_G}{T_f} = x_s G$$
 i.e. with gain
oise $\overline{y_n^2} = S_b \cdot \frac{T_G}{T_f^2} = \frac{S_b}{T_G} \cdot \left(\frac{T_G}{T_f}\right)^2 = \frac{S_b}{T_G} \cdot G^2 =$

$$G = \frac{T_G}{T_f} <<1$$

$$= \frac{S_b}{2T_n} \frac{2T_n}{T_G} G^2 = \overline{x_n^2} \cdot \frac{2T_n}{T_G} \cdot G^2$$

$$G = \frac{T_G}{T_f} <<1$$

Signal-to-noise ratio

$$\left(\frac{S}{N}\right)_{y} = \frac{y_{s}}{\sqrt{\overline{y_{n}}^{2}}} = \frac{x_{s}}{\sqrt{\overline{x_{n}}^{2}}} \cdot \sqrt{\frac{T_{G}}{2T_{n}}} = \left(\frac{S}{N}\right)_{x} \cdot \sqrt{\frac{T_{G}}{2T_{n}}}$$

NB: the output signal increases as T_G and the noise as $\sqrt{T_G}$, therefore the S/N increases as the square root of the gate time $\sqrt{T_G}$

WERN IMPORTAN

Output Signal and Noise of Gl



GI compared to other LPF

Fair comparison between different LPF with different DC gain G can be made by considering the value of the **filtered noise referred to the input** of the filter (and the input signal). This is equivalent to consider the **output with unity DC gain** (if necessary, by considering to add further gain stages).

For a GI this noise is

$$\left(\overline{x_n^2}\right)_{GI} = \frac{\left(\overline{y_n^2}\right)_{GI}}{G^2} = \frac{S_b}{T_G}$$

For a constant-parameter RC (inherently with G=1) that filters the same wide-band noise S_b it is

$$\left(\overline{x_n^2}\right)_{RC} = \left(\overline{y_n^2}\right)_{RC} = \frac{S_b}{2RC}$$

Therefore, as concerns the S/N obtained for input DC signals accompanied by wide-band noise, GI and RC integrator are equivalent if

$$T_G = 2RC$$

GI and equivalent RC-integrator



We consider here filters with equal DC gain of unity, hence with equal output signal. With wide-band input noise S_b the output noise is

$$\overline{y^2} = S_b \cdot k_{mmw} \ (0)$$

therefore, GI and RC have equal output noise if

$$T_G = 2RC$$

Signal Recovery, 2022/2023 – LPF-2

Ivan Rech

GI and equivalent RC-integrator



With $T_G = 2RC$ they are equivalent for:

- the S/N obtained with wide-band noise and DC signal input
- the attenuation of high-frequency disturbances in general **However:**
- The GI has zeros of $W_G(f)$ at $f_k = k/T_G$ that can be exploited to cancel specific disturbances at known frequencies (radio frequencies or mains frequency and harmonics)

