


## COURSE OUTLINE


- Introduction
- Signals and Noise
- **Filtering: OPF2 Optimum Filtering 2**
- Sensors and associated electronics

- High impedance sensors and low-noise preamplifiers
- Noise whitening filter
- Matched filter
- Practical approximations of the optimum filtering
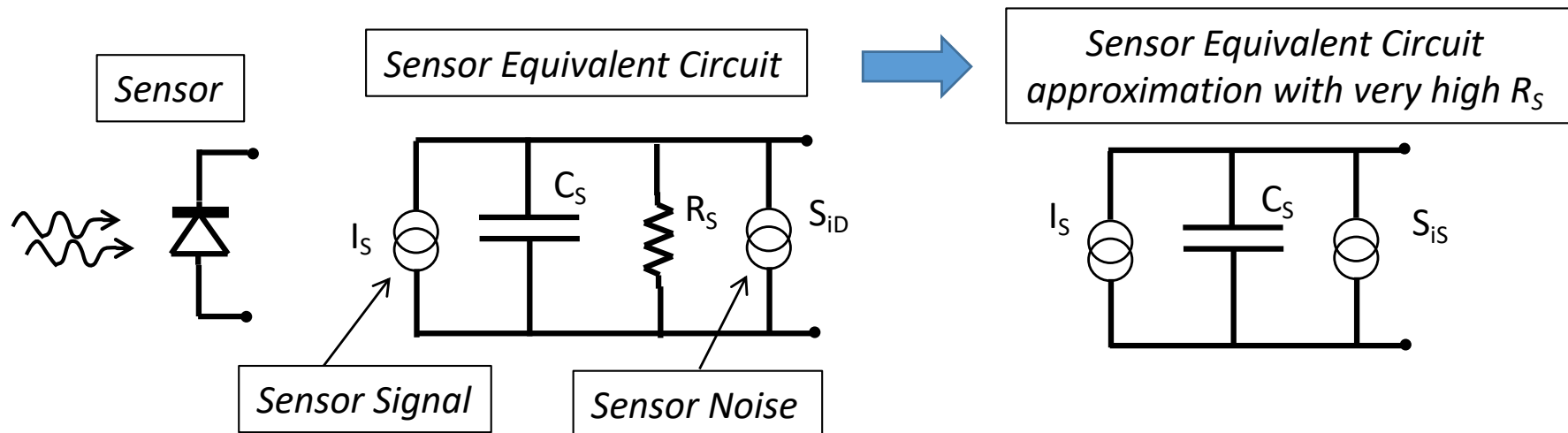
# High Impedance Sensors and Low-Noise Preamplifiers

- Let us consider sensors that are seen by the circuits connected to their terminals as generators of current signals with high internal impedance (typically a small capacitance  $C_S$  with a high resistance  $R_S$  in parallel)
- **Typical examples are:** p-i-n junction photodiodes and other photodetectors (CCDs, vacuum tube photodiodes, etc.); piezoelectric Force Sensors in quartz or other piezoelectric ceramic materials
- They have internal noise sources (e.g. shot current noise of a junction reverse current) modeled by a current noise generator in parallel to the signal generator



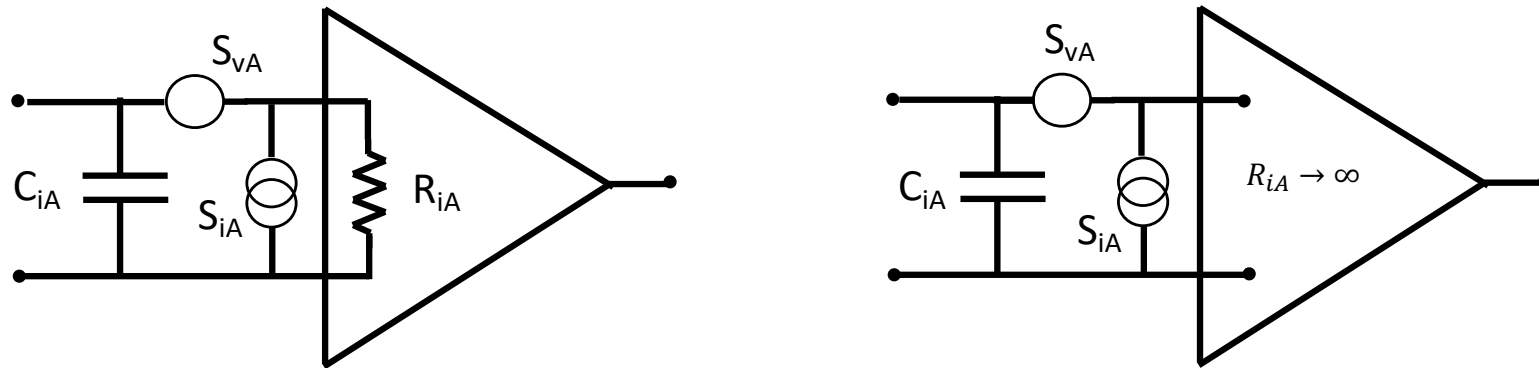

Preamplifier equivalent circuit




Approximation with very high  $R_{iA}$

- $R_{iA}$  = **true physical resistance** between the input terminals (**NOT the dynamic input resistance modified by the feedback in the amplifier**; e.g. not the low dynamic resistance of the virtual ground of an operational amplifier)
- Besides shot noise of bias currents, the  $S_{iA}$  includes Johnson resistor noise of  $R_{iA}$

$$S_{iR} = \frac{4kT}{R_i}$$

- The current noise directly faces the sensor current signal  $I_S$   
**if  $R_{iA}$  is small the  $S_{iR}$  is overwhelming** (e.g. with  $R_{iA} = 50 \Omega$  it is  $\sqrt{S_{iR}} \approx 18 \text{ pA}/\sqrt{\text{Hz}}$ ) and other components of  $\sqrt{S_{iA}}$  are much lower (about  $1 \text{ pA}/\sqrt{\text{Hz}}$  or lower)
- Conclusion: for **low-noise** operation of **high-impedance sensors**, it is **mandatory to employ a preamplifier with high input resistance  $R_{iA}$**

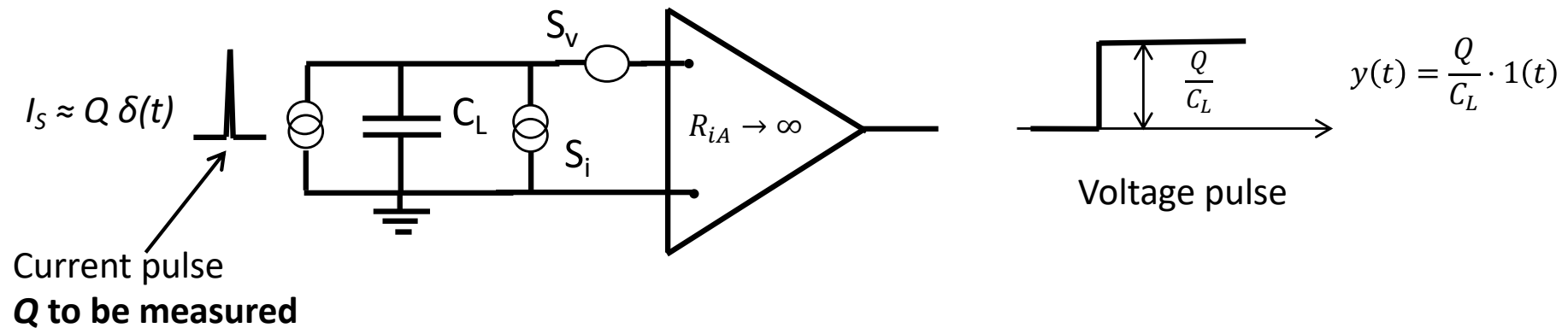Equivalent circuit of high-impedance Sensor and Preamplifier  
 (approximation valid for **very high** sensor resistance  $R_S \rightarrow \infty$ )



- $C_L = C_S + C_{iA}$  total capacitance load
- $S_V = S_{vA}$  voltage noise generator (wideband white spectrum)
- $S_i = S_{iD} + S_{iA}$  current noise generator (wideband white spectrum)

At the preamplifier output:

- The voltage noise spectrum  $S_n$  has two components, it is **NOT white**

$$S_n(\omega) = S_V + \frac{S_i}{\omega^2 C_L^2}$$


- The voltage signal is a step with amplitude  $Q/C_L$

Crossing of the component defines  $\omega_{nc}$  Noise-Corner angular frequency

$$S_v = \frac{S_i}{C_L^2 \omega_{nc}^2} \quad \rightarrow \quad \boxed{\omega_{nc} = \frac{\sqrt{S_i}}{C_L \sqrt{S_v}}}$$

$T_{nc} = 1/\omega_{nc}$  Noise-Corner time constant
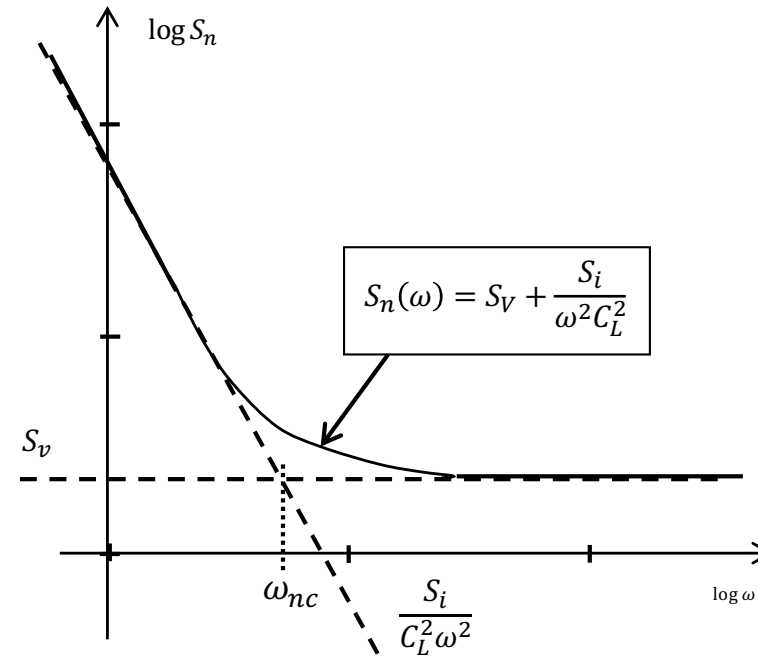
$$\boxed{T_{nc} = \frac{1}{\omega_{nc}} = \frac{\sqrt{S_v}}{\sqrt{S_i}} C_L}$$



$T_{nc}$  and  $\omega_{nc}$  are fundamental parameters of the optimum filter: we will see that  $T_{nc}$  rules the duration of the filter weighting and  $\omega_{nc}$  the filter bandlimit

We can define the **Noise Corner resistance**

$$\boxed{R_{nc} = \frac{\sqrt{S_v}}{\sqrt{S_i}}} \quad \text{so that} \quad \boxed{T_{nc} = R_{nc} C_L}$$

- with  $\sqrt{S_v}$  a few  $nV/\sqrt{Hz}$  and  $\sqrt{S_i}$  ranging from a few 0,1 to 0,01  $pA/\sqrt{Hz}$   
 **$R_{nc}$  ranges from tens to hundreds of kOhms**
- with  $C_L$  from 0,1 pF to a few pF  
 **$T_{nc}$  ranges from a few nanoseconds to some hundreds of nanoseconds**

# Noise whitening filter



# Noise-Whitening Filter

The noise spectrum has

- a pole at  $\omega_p = 0$
- a zero at  $\omega_z = \omega_{nc} = 1/T_{nc}$

$$S_n(\omega) = S_V \left( 1 + \frac{S_i}{\omega^2 S_V C_L^2} \right) = S_V \left( 1 + \frac{1}{\omega^2 T_{nc}^2} \right) = S_V \frac{1 + \omega^2 T_{nc}^2}{\omega^2 T_{nc}^2}$$

The noise whitening filter  $H_{nw}$  must



- cancel the pole with a zero at  $\omega = 0$
- cancel the zero with a pole at  $\omega = \omega_{nc} = 1/T_{nc}$

$$|H_{nw}(\omega)|^2 = \frac{\omega^2 T_{nc}^2}{1 + \omega^2 T_{nc}^2}$$

It is a simple high-pass filter


$$H_{nw}(\omega) = \frac{j\omega R_w C_w}{1 + j\omega R_w C_w}$$

with  $R_w C_w = T_{nc}$

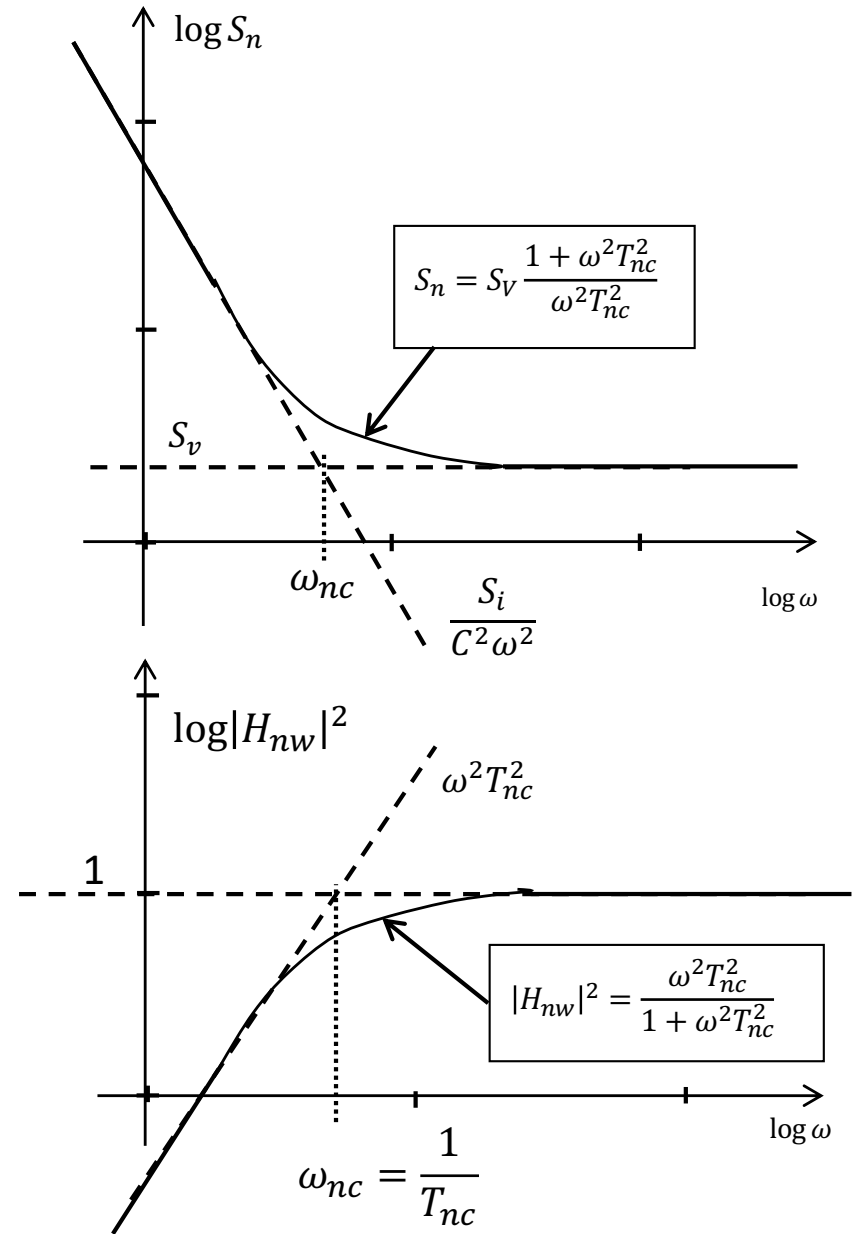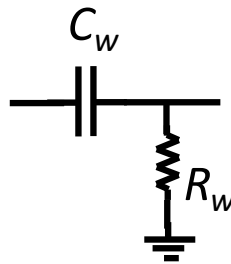


# Action of the Noise-Whitening Filter

Simple high-pass CR filter

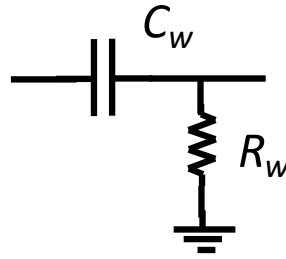


$$H_{nw}(s) = \frac{sR_w C_w}{1 + sR_w C_w}$$


with  $R_w C_w = T_{nc}$

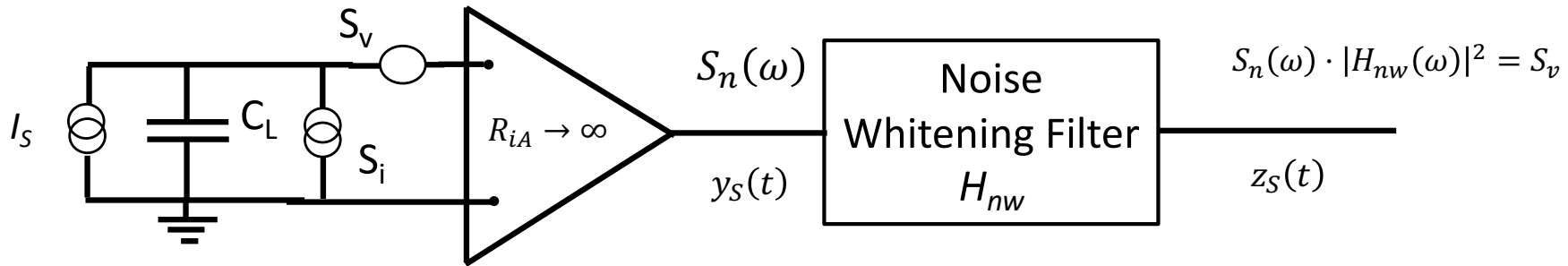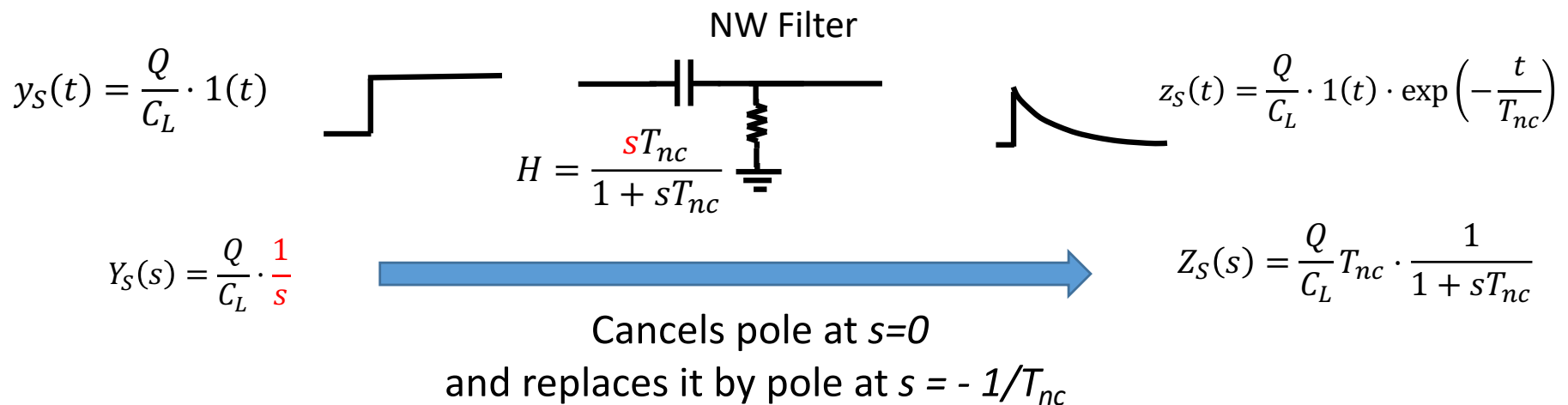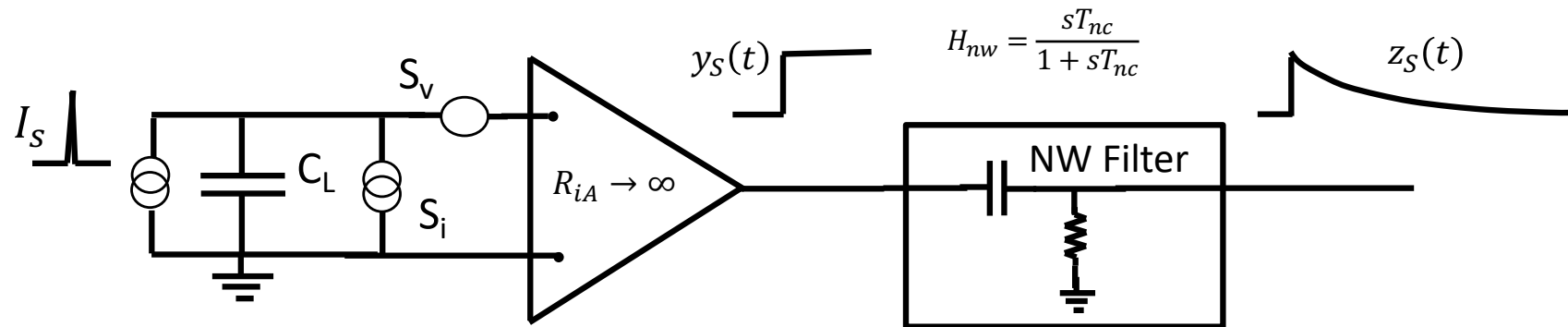
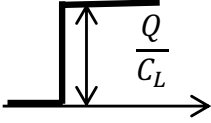
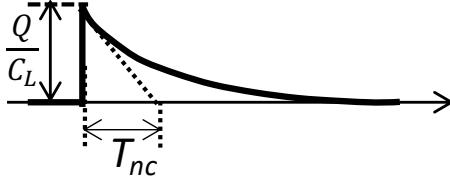


it makes **white** the noise at its **output**

and changes the signal into a short **exponential pulse with time-constant  $T_{nc}$**






| Input (current)   | Preamplifier Output (voltage)  | NW Filter Output (voltage)   |
|---|--|--|
| $\delta$ - pulse<br> | Step pulse<br> | Exponential pulse<br> |
| $I_s(t) = Q \cdot \delta(t)$  | $y_S(t) = \frac{Q}{C_L} \cdot 1(t)$  | $z_S(t) = \frac{Q}{C_L} \cdot 1(t) \cdot \exp\left(-\frac{t}{T_{nc}}\right)$                             |
| $I_s(s) = Q$  | $Y_S(s) = \frac{Q}{C_L} \cdot \frac{1}{s}$   | $Z_S(s) = \frac{QT_{nc}}{C_L} \frac{1}{1 + sT_{nc}}$   |

The **matched** filter has to be tailored to the signal at the whitening filter output, i.e. it must have **weighting function exponential with time constant  $T_{nc}$**

# Matched Filter

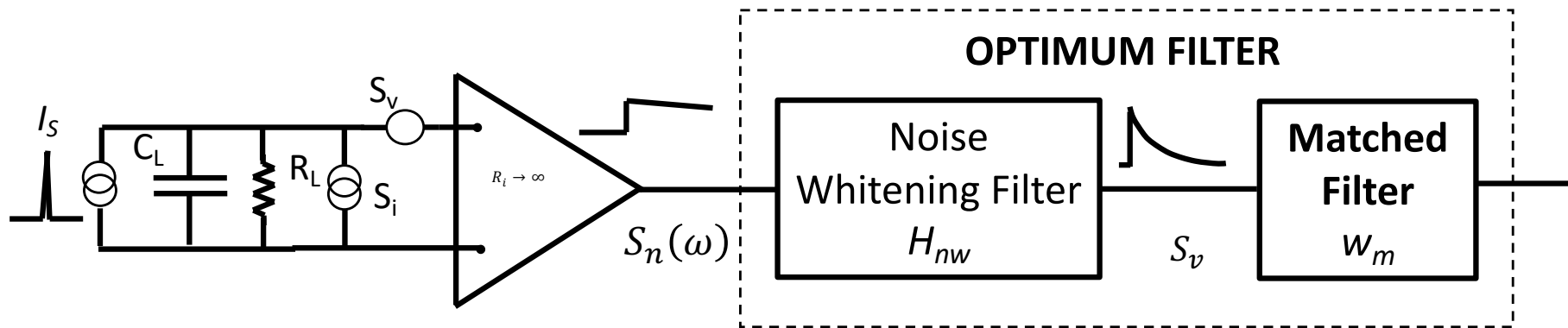

In the case with finite load resistance  $R_L$  the whitening filter is different but the output signal produced is the same as with  $R_L \rightarrow \infty$

$$z_S(t) = \frac{Q}{C_L} \cdot 1(t) \cdot \exp\left(-\frac{t}{T_{nc}}\right)$$

Therefore, the matched filter is the same in the two cases

$$w_M = 1(t) \cdot \frac{1}{T_{nc}} \exp\left(-\frac{t}{T_{nc}}\right)$$

and gives the same result

$$\left(\frac{S}{N}\right)_{opt}^2 = \frac{A^2}{S_v} \cdot \int_{-\infty}^{\infty} b^2(\alpha) d\alpha \quad \longrightarrow \quad \left(\frac{S}{N}\right)_{opt}^2 = \frac{Q^2 T_{nc}^2}{C_L^2 S_v} \int_{-\infty}^{\infty} w_m^2(\alpha) d\alpha = \frac{Q^2}{C_L^2} \frac{1}{2} \frac{T_{nc}}{S_v}$$

At the output of the optimum filter (i.e. of the matched filter) we have

$$\text{Signal} \quad s_o = \int_0^{\infty} z_s(\alpha) w_m(\alpha) d\alpha = \frac{Q}{C_L} \frac{1}{T_{nc}} \int_0^{\infty} \exp\left(-\frac{2\alpha}{T_{nc}}\right) d\alpha = \frac{1}{2} \frac{Q}{C_L}$$


$$\text{Noise} \quad \sqrt{n_o^2} = \sqrt{S_v} \cdot \sqrt{k_{ww}(0)} = \sqrt{S_v} \frac{1}{T_{nc}} \sqrt{\int_0^{\infty} \exp\left(-\frac{2\alpha}{T_{nc}}\right) d\alpha} = \sqrt{\frac{S_v}{2T_{nc}}}$$

$$\text{S/N} \quad \boxed{\frac{s_o}{\sqrt{n_o^2}} = \frac{1}{2} \frac{Q}{C_L} \sqrt{\frac{2T_{nc}}{S_v}}}$$

- The optimum filter theory specifies **what is the best S/N physically obtainable** and the kind of filter required for attaining it
- The optimum filter can be implemented in reality, but the filter design turns out to be quite **complex**
- Furthermore, the optimum filter takes **infinite time** (after the signal onset) to complete its action, which is not acceptable in practice
- It is possible, however, to consider and evaluate fairly simple filters that **approximate the optimum** filter and closely approach its performance
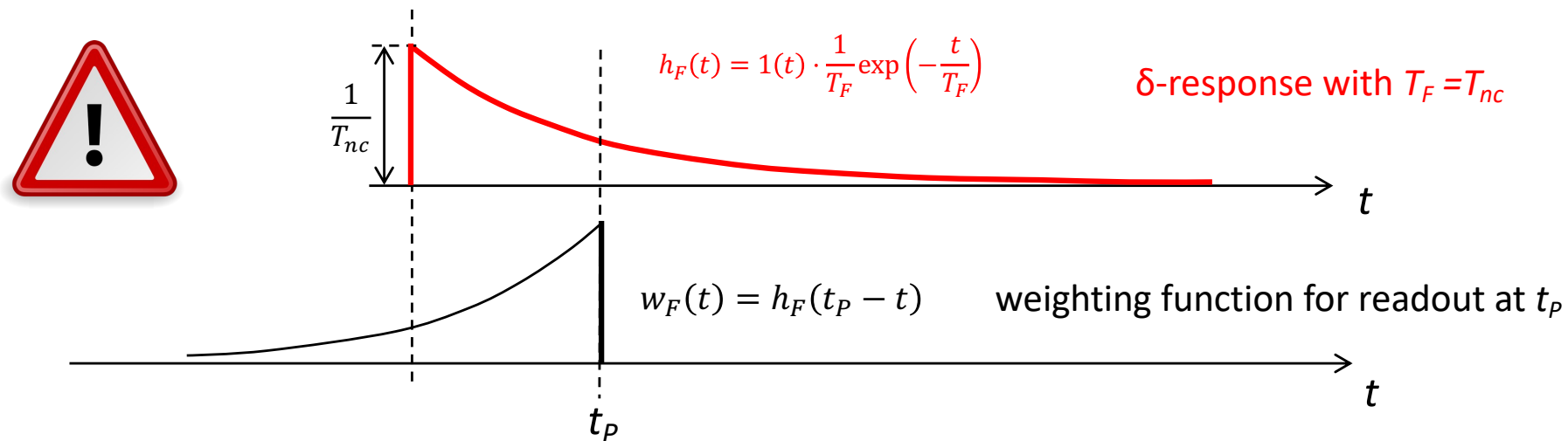
# Practical approximations of the optimum filtering


- The features of the matched filter weighting function observed in time and in frequency point out that it is a **low-pass filter**
- A simple **RC integrator** (single-pole low-pass filter) can be an **approximation** of the matched filter. With  $RC = T_{nc}$  its  $\delta$ -response  $h_F(t)$  is identical to the weighting function  $w_M(t)$  of the matched filter.
- **The RC weighting  $w_F(t)$  has the same shape as  $w_M(t)$  of the matched filter, but it's not fully correct because it is reversed in time!**



- **Noise filtering is equal to the matched filter**, since it is unaffected by time-inversion; the output is white noise with band-limit set by a simple pole with time-constant  $T_F$ .
- **Signal filtering is different** from the matched filter, since it is modified by time-inversion


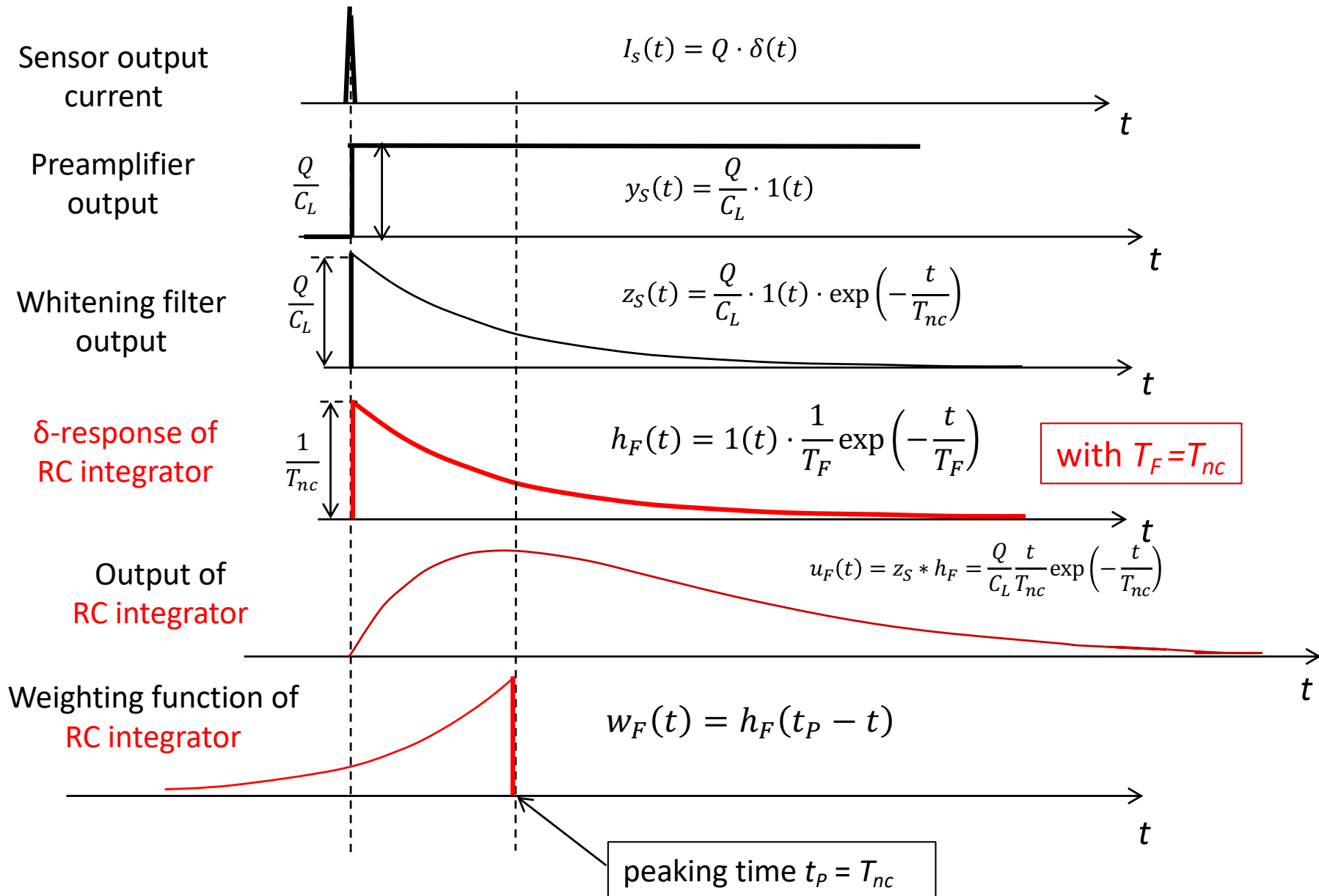
# RC integrator Approximation of the Matched Filter



# RC integrator Approximation compared to the Optimum Filter

The RC output signal waveform is  $u_F(t) = \frac{Q}{C_L T_{nc}} \exp\left(-\frac{t}{T_{nc}}\right)$

Signal peak value (at  $t = T_{nc}$ )  $s_F = u_F(T_{nc}) = \frac{1}{e} \frac{Q}{C_L}$

Noise  $\sqrt{n_F^2} = \sqrt{S_v} \cdot \sqrt{k_{hh}(0)} = \sqrt{\frac{S_v}{2T_{nc}}}$

S/N  $\frac{s_F}{\sqrt{n_F^2}} = \frac{1}{e} \frac{Q}{C_L} \sqrt{\frac{2T_{nc}}{S_v}}$

Comparing the RC approximation with the ideal optimum filter system we see that

$s_F = \frac{2}{e} s_o \approx 0,736 \cdot s_o$  the signal is lower

$\sqrt{n_F^2} = \sqrt{n_o^2}$  the noise is equal

$SNR_F = \frac{2}{e} \eta_o \approx 0,736 \cdot SNR_o$  the S/N is lower

the performance of the filter system with RC approximation of matched filter is about 27% worse than the absolute optimum.

Note that the loss is due to bad exploitation of the signal