

(NB: see text also on the other side of the sheet)

**Problem 1**

<p><b>Pulse signal</b>                  Exponential signal  <math>V_P</math> variable pulse amplitude  <math>B</math> constant                  Sync available  <math>\tau = 10\mu s</math>  <b>Preamplifier</b>  <math>S_V^{1/2} = 20nV/Hz^{1/2}</math> white noise spectral density (unilateral)  <math>f_{pa} = 50 MHz</math> upper band-limit</p>	
---	--

- A) Considering only the exponential signal, with  $B=0$ , select the best Gated Integrator in order to obtain the minimum signal that can be detected with this solution. Describe each step quantitatively.
- B) Consider now to have an **unknown background B**. Discuss if and how it is possible to extract the pulse amplitude information. Compare the results with the result obtained in point A and discuss the impact of the new proposed solution on the minimum signal that can be detected.
- C) Consider now the same signal but with a repetition rate of 1kHz and the amplitude  $V_p$  that slowly changes in the time scale of a few seconds. How it is possible to use this information to reduce the minimum detectable signal? Propose a solution, select the parameters and quantitatively evaluate the results that can be obtained.
- D) Explain in detail the concept, the weighting function and the low frequency cut-off of the CDS (Correlated Double Sampling). Describe the effect of the CDS on band-limited white noise with a time domain analysis.

(NB: see text also on the other side of the sheet)

**Problem 2**

	<p><b>PREAMPLIFIER</b></p> <p><math>S_V^{1/2} = 20nV/Hz^{1/2}</math> white noise power density (unilateral)</p> <p>1/f frequency corner: 10KHz</p> <p><math>f_{pa} = 50 MHz</math> upper band-limit</p>
--	---

We want to measure the temperature of a small apparatus using a PT100 sensor with a Wheatstone bridge configuration. The resistance of the sensor at the desired temperature is 120 Ohm and the bias of the bridge is 25mV.

- A) Assuming that the temperature signal can change on the time scale of 1 second, evaluate the minimum variation of temperature that it is possible to measure. Additional analog or digital stages can be used, if needed.
- B) Consider now a sinusoidal bias of the bridge featuring the same amplitude of the steady state signal previously used (i.e. 25mV) and frequency 100 kHz. **It is possible to sample the output of the bridge only 100 times without using any additional filter.** Select the time instants of the sampling points and evaluate the minimum detectable signal with the proposed solution.
- C) Consider now that it is possible to use either a Lock-in Amplifier or a resonant filter. Discuss which filter is more suitable in this case, select its parameters and evaluate the minimum signal that can be detected with the proposed solution.
- D) Discuss if and how it is possible to use PN junctions instead of PT100 as temperature sensors in this application.